

EE1 Simple AC Circuit Analysis Examples

Professor Timothy Drysdale

February 25, 2020

We step through the analysis of two example circuits at single frequency

- series RC
- parallel RL

Series RC

Let

$$\omega = 200\pi \quad (1)$$

$$V_{ac} = 200e^{j\omega t} \quad (2)$$

$$R = 100\Omega \quad (3)$$

$$C = 20\mu F \quad (4)$$

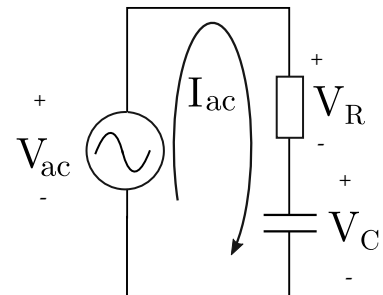


Figure 1: Series RC circuit

What else do we know?

•

$$Z_C = \frac{1}{j\omega C}$$

•

$$V = IZ$$

- voltages around a loop must sum to zero, at all times
- the same current flows in all components of a simple series circuit

What do we not know?

- the current flowing in the supply/resistor/capacitor
- the voltage across the resistor
- the voltage across the capacitor

One approach is to calculate the total impedance of the circuit at a single frequency, and do all the book work numerically at a single frequency.

$$Z_T = Z_R + Z_C \quad (5)$$

$$= R + \frac{1}{j\omega C} \quad (6)$$

$$= 100 - j80 \quad (7)$$

Then we can calculate the current

$$I_{ac} = \frac{V}{Z_T} \quad (8)$$

$$= \frac{200}{100 - j80} \quad (9)$$

$$= \frac{200(100 + j80)}{(100 - j80)(100 + j80)} \quad (10)$$

$$= \frac{20 \times 10^3 + j16 \times 10^3}{10 \times 10^3 + 6.4 \times 10^3} \quad (11)$$

$$= 1.22 + j0.98A \quad (12)$$

we multiply by the complex conjugate $(100 + j80)$ to make the denominator real

Note that we drop the exponential part of the voltage for convenience. We know it is there, and we'll add it back in later. What does our result mean? We still need to work out the magnitude $|I_{ac}|$ and phase $\angle I_{ac}$. The magnitude is

$$|I_{ac}| = |1.22 + j0.98| \quad (13)$$

$$= \sqrt{1.22^2 + 0.98^2} \quad (14)$$

$$= 1.56A. \quad (15)$$

We can double check our value for I_{ac} by calculating the magnitude of the impedance first

$$|I_{ac}| = \frac{V}{|Z_T|} \quad (16)$$

$$= \frac{200}{\sqrt{100^2 + 80^2}} \quad (17)$$

$$= \frac{200}{128.1} \quad (18)$$

$$= 1.56A \quad (19)$$

which is the same as before.

The phase is

$$\angle I_{ac} = \arctan \frac{\text{Im}\{I_{ac}\}}{\text{Re}\{I_{ac}\}} \quad (20)$$

$$= \arctan \frac{0.98}{1.22} \quad (21)$$

$$= 38.8^\circ \quad (22)$$

We can see the results on a phasor diagram of Figure 2. This is only a qualitative representation - you do not need to draw the phasors to scale in the exam because you will be drawing the phasor diagram *before* you've worked out any values!

We should calculate the voltage across the components. The volt-

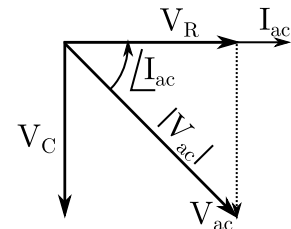


Figure 2: Series RC circuit phasor diagram

age across the capacitor is

$$V_C = I_{ac} Z_L \quad (23)$$

$$= 1.22 + j0.98 \times -j80 \quad (24)$$

$$= 78.4 - j97.6 \quad [\text{V}] \quad (25)$$

$$V_R = I_{ac} Z_R \quad (26)$$

$$= 1.22 + j0.98 \times 100 \quad (27)$$

$$= 122 + j98 \quad [\text{V}] \quad (28)$$

We can check that these sum to give V_{ac}

$$78.4 - j97.6 + 122 + j98 = 200.4 + j0.4 \quad [\text{V}] \quad (29)$$

which is just slightly out due to some rounding error carried through from earlier.

That's a basic solution done and dusted. As we will later see with filters, it can sometimes be convenient to work out the result for the general case, and substitute in numbers as you need them. We'll try that now, just to see what it is like. So let's calculate the current for any frequency and voltage

$$I_{ac} = \frac{V}{Z_T} \quad (30)$$

$$= \frac{V}{R + \frac{1}{j\omega C}} \quad (31)$$

$$= \frac{jV\omega C}{1 + j\omega RC} \quad (32)$$

The magnitude of the current is

$$|I| = \left| \frac{jV\omega C}{1 + j\omega RC} \right| \quad (33)$$

$$= \frac{|jV\omega C|}{|1 + j\omega RC|} \quad (34)$$

$$= \frac{V\omega C}{\sqrt{1 + (\omega RC)^2}} \quad (35)$$

To find the phase of the current, we need to first make the denominator real so we can separate out the real and imaginary parts.

We multiply by the complex conjugate

$$I_{ac} = \frac{jV\omega C}{1 + j\omega RC} \frac{1 - j\omega RC}{1 - j\omega RC} \quad (36)$$

$$= \frac{V\omega C(1j - \omega RC)}{1 + (\omega RC)^2} \quad (37)$$

$$(38)$$

Now the phase can be found as

$$\angle I_{ac} = \arctan \frac{\text{Im}\{I_{ac}\}}{\text{Re}\{I_{ac}\}} \quad (39)$$

$$= \arctan \frac{1}{-\omega RC} \quad (40)$$

We can check these equations by substituting in the parameters and checking we get the same answers as before. The magnitude of the current is

$$|I| = \frac{V\omega C}{\sqrt{1 + (\omega RC)^2}} \quad (41)$$

$$= \frac{200 \cdot 200\pi \cdot 20 \times 10^{-6}}{\sqrt{1 + (200\pi \cdot 100 \cdot 20 \times 10^{-6})^2}} \quad (42)$$

$$= 1.56 \quad [\text{A}] \quad (43)$$

The phase of the current is

$$\angle I_{ac} = \arctan \frac{1}{-\omega RC} \quad (44)$$

$$= \arctan \frac{1}{-200\pi \cdot 100 \cdot 20 \times 10^{-6}} \quad (45)$$

$$= 38.5^\circ \quad (46)$$

which is ever so slightly (0.3°) different due to the rounding error in our earlier numerical calculations.

Parallel RL

Let

$$\omega = 2\pi \times 10^5 \quad (47)$$

$$V_{ac} = 250e^{j\omega t} \quad (48)$$

$$R = 1000\Omega \quad (49)$$

$$L = 1\text{mH} \quad (50)$$

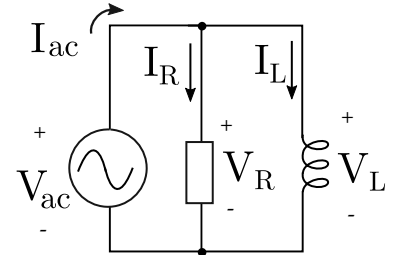


Figure 3: Parallel RL circuit

What else do we know?

-

$$Z_L = j\omega L$$

-

$$X_L = \omega L$$

-

$$V = IZ$$

- currents into a node equal currents out of a node, at all times
- voltages across parallel branches are equal, at all times

What do we not know?

- the current flowing in the resistor
- the current flowing in the inductor
- the current flowing in the supply

We know that the voltage must be the same across each branch, so we can calculate the magnitude of the component currents separately and then add vectorially to get the supply current, as shown in Figure 4. The magnitude of the resistor current is

$$|I_R| = \frac{V}{R} \quad (51)$$

$$= \frac{250}{1000} \quad (52)$$

$$= 0.25 \quad [\text{A}] \quad (53)$$

The magnitude of the inductor current is

$$|I_L| = \frac{V}{X_L} \quad (54)$$

$$= \frac{250}{2\pi \times 10^5 \cdot 1 \times 10^{-3}} \quad (55)$$

$$= 0.40 \quad [\text{A}] \quad (56)$$

The supply current is

$$I_{ac} = I_R + I_L \quad (57)$$

$$= |I_R| - j|I_L| \quad (58)$$

$$= 0.25 - j0.40 \quad [\text{A}] \quad (59)$$

where we use a $-j$ because CIVIL tells us the voltage must lead the current in the inductor.

Or, taking the same approach as last time, and calculating the total impedance we find

$$Z_T = Z_R // Z_L \quad (60)$$

$$= \frac{j\omega RL}{R + j\omega L} \quad (61)$$

$$= 283 + 450j \quad [\Omega] \quad (62)$$

giving the current as

$$I_{ac} = \frac{V}{Z_T} \quad (63)$$

$$= \frac{250}{283 + j450} \quad (64)$$

$$= 0.25 - j0.40 \quad [\text{A}] \quad (65)$$

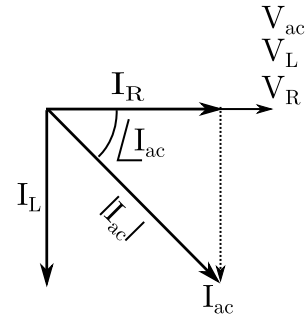


Figure 4: Parallel RL circuit phasor diagram

which agrees with our earlier result.

The magnitude of the supply current is

$$|I_{ac}| = |0.25 - j0.40| \quad (66)$$

$$= \sqrt{0.25^2 + 0.40^2} \quad (67)$$

$$= 0.47 \quad [\text{A}] \quad (68)$$

The phase of the supply current is

$$\angle I_{ac} = \arctan \frac{\text{Im}\{I_{ac}\}}{\text{Re}\{I_{ac}\}} \quad (69)$$

$$= \arctan \frac{-0.40}{0.25} \quad (70)$$

$$= -58^\circ \quad (71)$$

The waveforms are shown in Figure ?? as if they were on the oscilloscope screen.

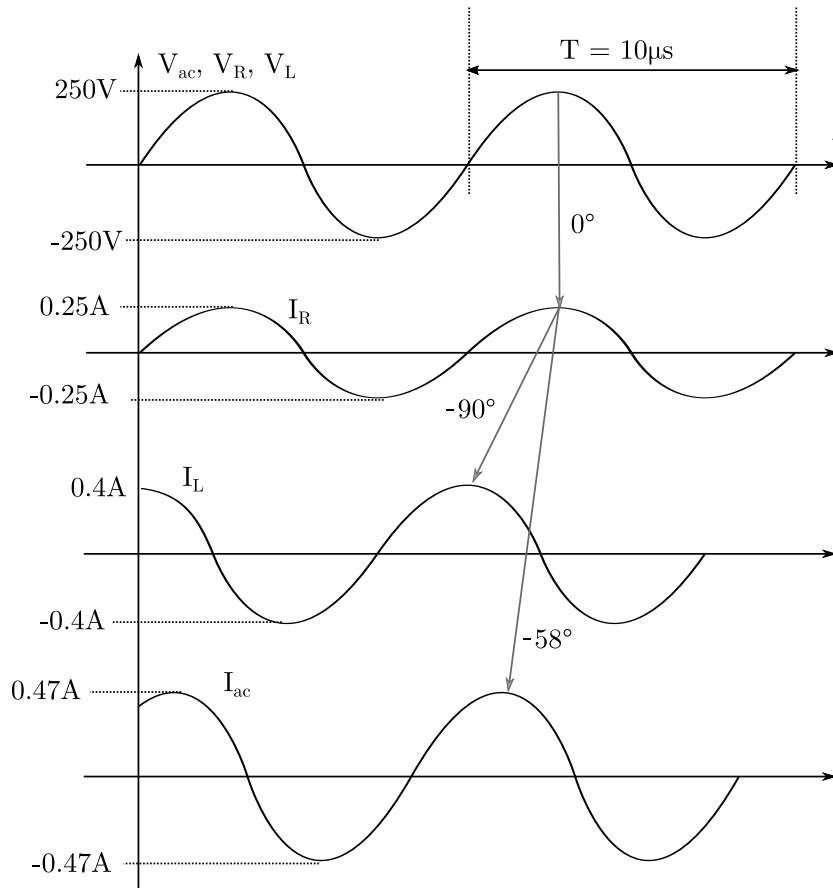


Figure 5: Waveforms for the parallel RL circuit